



# Amateur Radio Technician Exam Preparation



# Amateur Radio Technician Exam Prep Course

## Module 3

### Electricity, Components, and Circuits

- 3.1 Electricity
- 3.2 Components and Units
- 3.3 Radio Circuits

# Fundamentals of Electricity


- Radios are powered by electricity and radio signals are a form of electrical energy
- A basic understanding of how we control electricity allows you to better install and operate your radio
- Electrical charge can be positive or negative
  - Opposite charges attract each other (like charges repel)
- Electrical current is the flow of *electrons*
  - Electrons are negatively-charged atomic particles, usually surrounding an atom's positively-charged nucleus of protons (positive) and neutrons (neutral – no charge)
  - Electrons move in response to an *electromotive force* and can move independently of atoms

# Basic Electrical Concepts

- Current: the movement of electrons, measured in *amperes* (**A**) by an *ammeter*, and represented by **I** (capital letter “i”) in formulas
- Voltage: the amount of electromotive force (emf), also called electrical potential, measured in *volts* (**V**) by a *voltmeter*, represented by **E** or **V** in formulas
- Resistance: the opposition to the movement of electrons, measured in *ohms* (**Ω**) by an *ohmmeter* and represented by **R** (sometimes  $\Omega$  in scientific publications) in formulas
- Resistance is like friction and turns electrical energy into heat when current flows
- *Conductors* permit current flow (low resistance) and *insulators* block current flow (high resistance)
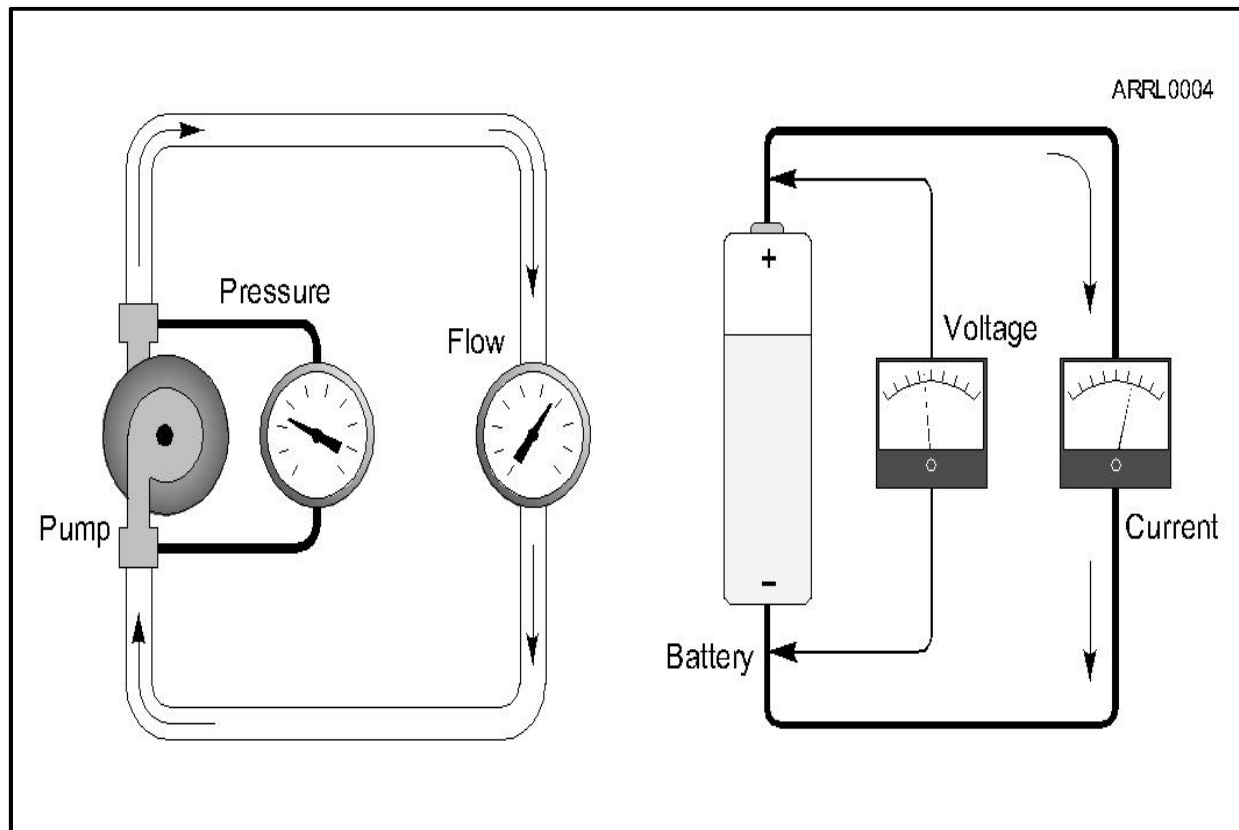
# Basic Electrical Concepts (cont.)

- The flow of water through a pipe is a good analogy to understand the three characteristics of electricity and how they are related



# Basic Electrical Concepts (cont.)

- *Polarity* refers to the convention that determines which voltages are positive and negative
- Voltage from a *source* of electrical energy causes current to flow
- *Resistance* is a material's opposition to the flow of current
- Voltage, current, and resistance affect each other
  - For example, higher voltage (bigger push) causes more current (more flow)

# PRACTICE QUESTIONS

**Electrical current is measured in which of the following units?**

- A. Volts
- B. Watts
- C. Ohms
- D. Amperes



**What is the name for the flow of electrons in an electric circuit?**

- A. Voltage
- B. Resistance
- C. Capacitance
- D. Current

**What is the electrical term for the force that causes electron flow?**

- A. Voltage
- B. Ampere-hours
- C. Capacitance
- D. Inductance

# Which of the following describes alternating current?

- A. Current that alternates between a positive direction and zero
- B. Current that alternates between a negative direction and zero
- C. Current that alternates between positive and negative directions
- D. All these answers are correct

# Which instrument would you use to measure electric potential?


- A. An ammeter
- B. A voltmeter
- C. A wavemeter
- D. An ohmmeter

# Which instrument is used to measure electric current?

- A. An ohmmeter
- B. An electrometer
- C. A voltmeter
- D. An ammeter
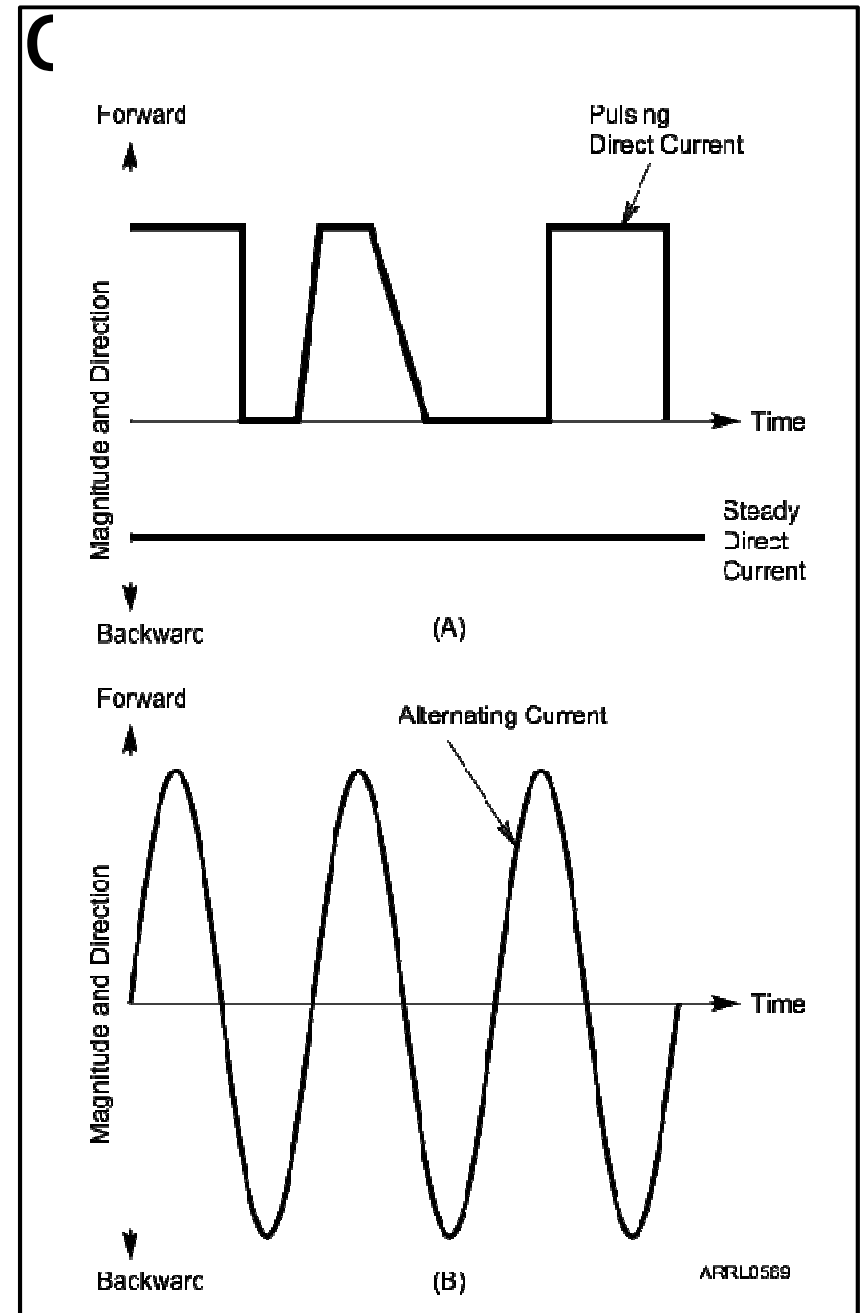
# The Two Kinds of Current


- Current that flows in only one direction, is called *direct current* (DC)
  - Batteries are a common source of DC
- Current that flows in one direction then in the opposite direction is called *alternating current* (AC)
  - Household current is AC



# Current Flow

- A *circuit* is any path through which current can flow
- Electrical circuits are made from *components* and the connections between them
- If two or more components are connected in a circuit so that the same current must flow through all of them, that is a *series* circuit
- A *short circuit* is a direct connection between two points in a circuit
- An *open circuit* is made by breaking a current


# Series Circuit

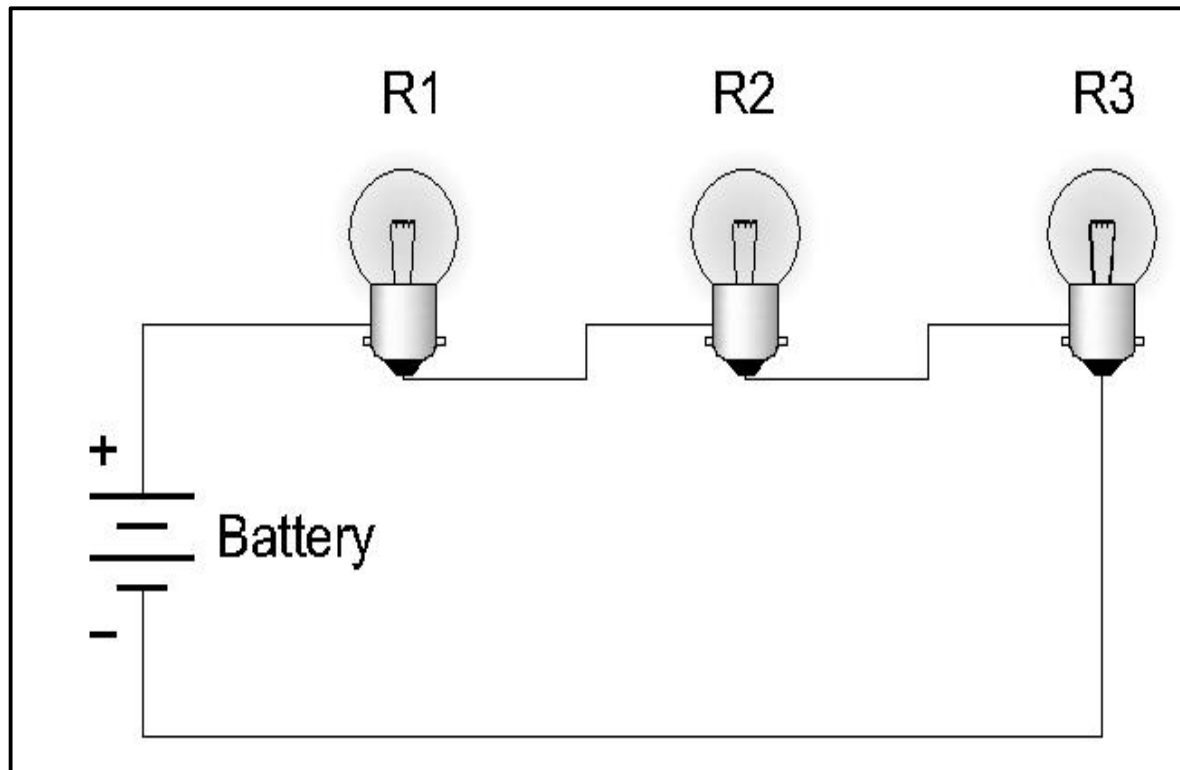

Same **CURRENT** at all points in the circuit. Series circuits provide one and only one path for current flow.



# Parallel Circuit

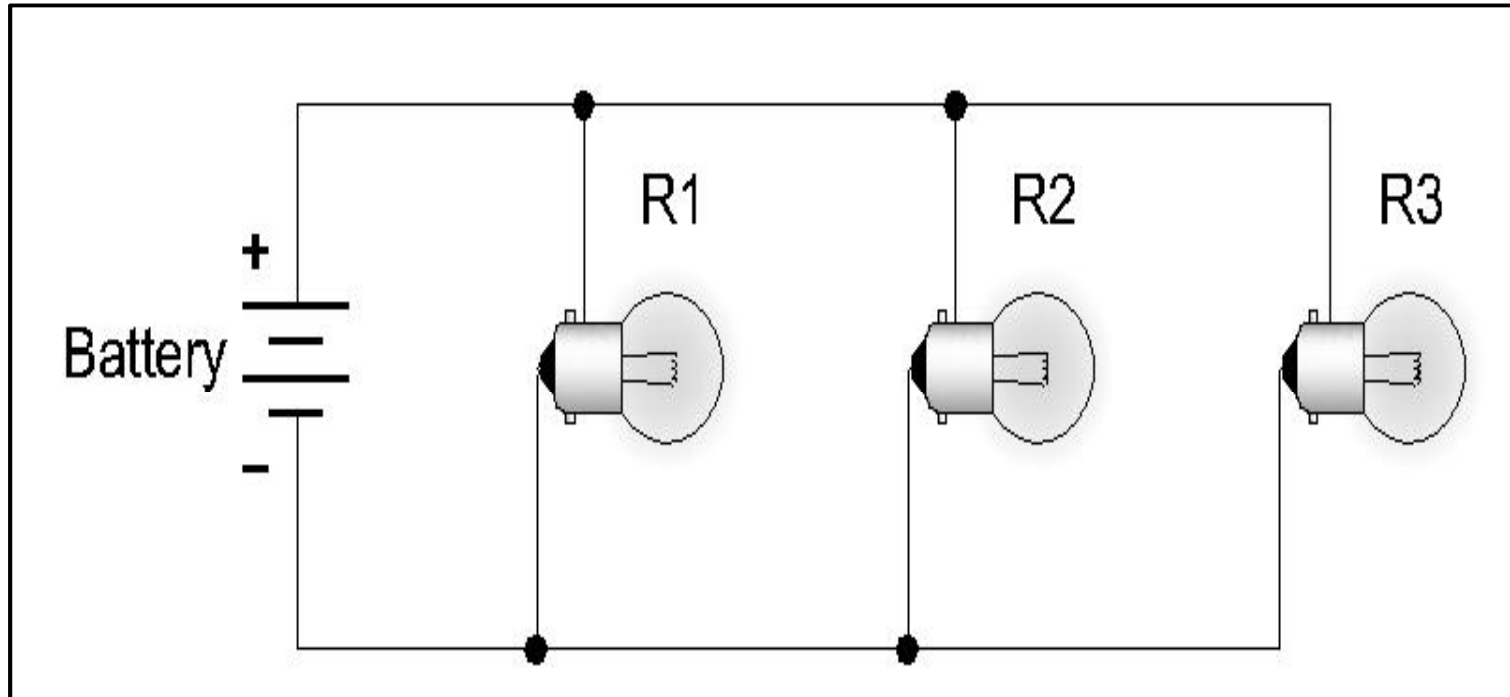

Same **VOLTAGE** at all parts of the circuit. Parallel circuits provide multiple paths for current flow.

# PRACTICE QUESTIONS

**In which type of circuit is DC current the same through all components?**

- A. Series
- B. Parallel
- C. Resonant
- D. Branch

**In which type of circuit is voltage the same across all components?**

- A. Series
- B. Parallel
- C. Resonant
- D. Branch

**How is a voltmeter connected to a component to measure applied voltage?**

- A. In series
- B. In parallel
- C. In quadrature
- D. In phase

**When configured to measure current, how is a multimeter connected to a component?**

- A. In series
- B. In parallel
- C. In quadrature
- D. In phase

# Multimeters

- The basic electrical test instruments are simple meters: voltmeters, ammeters, and ohmmeters
- So that a separate meter isn't needed for each parameter, the *multimeter* was invented
  - Short for “multifunction meter”
  - Measures all three electrical values of voltage, current, and resistance
  - Other names: *VOM* (volt-ohm meter) or *DVM* (digital volt meter)
- Ways meters are damaged ...

# PRACTICE QUESTIONS



## Which of the following can damage a multimeter?

- A. Attempting to measure resistance using the voltage setting
- B. Failing to connect one of the probes to ground
- C. Attempting to measure voltage when using the resistance setting
- D. Not allowing it to warm up properly

# Which of the following measurements are made using a multimeter?

- A. Signal strength and noise
- B. Impedance and reactance
- C. Voltage and resistance
- D. All these choices are correct

**What reading indicates that an ohmmeter is connected across a large, discharged capacitor?**

- A. Increasing resistance with time
- B. Decreasing resistance with time
- C. Steady full-scale reading
- D. Alternating between open and short circuit


**Which of the following precautions should be taken when measuring in-circuit resistance with an ohmmeter?**

- A. Ensure that the applied voltages are correct
- B. Ensure that the circuit is not powered
- C. Ensure that the circuit is grounded
- D. Ensure that the circuit is operating at the correct frequency

# Which of the following precautions should be taken when measuring high voltages with a voltmeter?

- A. Ensure that the voltmeter has very low impedance
- B. Ensure that the voltmeter and leads are rated for use at the voltages to be measured
- C. Ensure that the circuit is grounded through the voltmeter
- D. Ensure that the voltmeter is set to the correct frequency

# Ohm's Law

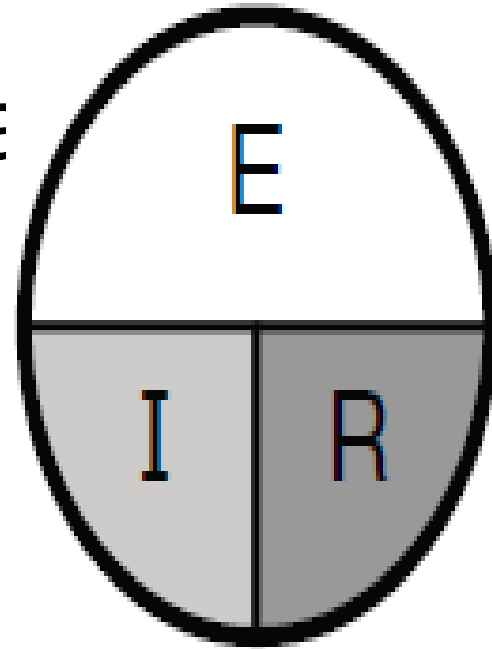


- **E** represents voltage
  - Units – volts (V)
- **I** represents current
  - Units – amperes (A)
- **R** represents resistance
  - Units – ohms ( $\Omega$ )

$$R = E / I$$
$$I = E / R$$
$$E = I \times R$$

Figure 3.5A — Simple diagram to help remember the Ohm's Law. If you know any two of the quantities, the equation to find the third — just cover up the unknown quantity. The positions of the remaining two symbols show if you have to multiply (side-


# Examples of how to use Ohm's Law

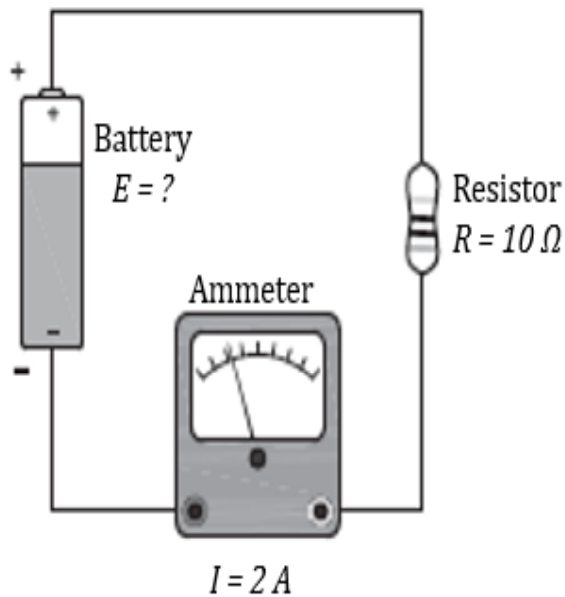

Given  $I = 2$  Amperes  
 $R = 10$  Ohms

Find:  $E$  (voltage)

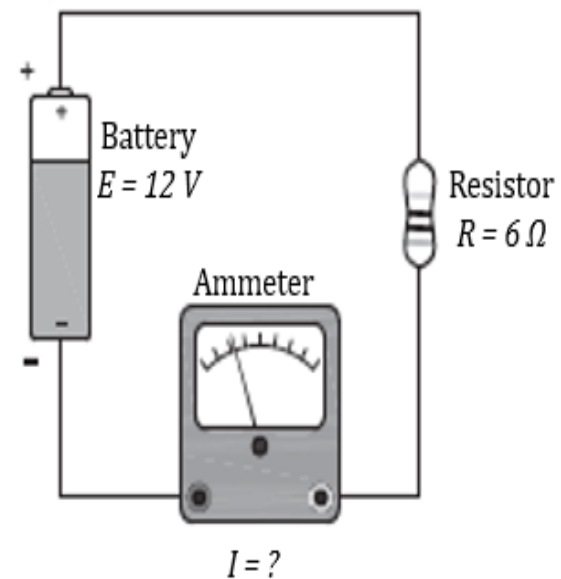$E = I \times R = 2 \times 10 = 20$  Volts  
Voltage Equals 20 Volts



Given  $E = 12$  Volts  
 $R = 6$  Ohms

Find:  $I$  (current)

$I = E / R = 12 / 6 = 2$  Amps

Current Equals 2 Amperes

# More Ohm's Law Examples

What is the resistance of a circuit in which a current of 3 amperes flows when connected to 90 volts?

$$R = E / I = 90 \text{ V} / 3 \text{ A} = 30 \Omega$$

What is the current in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?

$$I = E / R = 120 \text{ V} / 80 \Omega = 1.5 \text{ A}$$

What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?

$$E = I \times R = 0.5 \text{ A} \times 2 \Omega = 1 \text{ V}$$



# PRACTICE QUESTIONS

# What are the units of electrical resistance?

- A. Siemens
- B. Mhos
- C. Ohms
- D. Coulombs

# Why are metals generally good conductors of electricity?

- A. They have relatively high density
- B. They have many free electrons
- C. They have many free protons
- D. All these choices are correct

**Which of the following is a good electrical insulator?**

- A. Copper
- B. Glass
- C. Aluminum
- D. Mercury

**What formula is used to calculate current in a circuit?**

A.  $I = E \times R$

B.  $I = E / R$

C.  $I = E + R$

D.  $I = E - R$

**What formula is used to calculate voltage in a circuit?**

A.  $E = I \times R$

B.  $E = I / R$

C.  $E = I + R$

D.  $E = I - R$

**What formula is used to calculate resistance in a circuit?**

A.  $R = E \times I$

B.  $R = E / I$

C.  $R = E + I$

D.  $R = E - I$

**What is the resistance of a circuit in which a current of 3 amperes flows when connected to 90 volts?**

- A. 3 ohms
- B. 30 ohms
- C. 93 ohms
- D. 270 ohms



**What is the resistance of a circuit for which the applied voltage is 12 volts and the current flow is 1.5 amperes?**

- A. 18 ohms
- B. 0.125 ohms
- C. 8 ohms
- D. 13.5 ohms

**What is the resistance of a circuit that draws  
4 amperes from a 12-volt source?**

- A. 3 ohms
- B. 16 ohms
- C. 48 ohms
- D. 8 ohms

**What is the current in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?**

- A. 9600 amperes
- B. 200 amperes
- C. 0.667 amperes
- D. 1.5 amperes

**What is the current through a 100-ohm resistor connected across 200 volts?**

- A. 20,000 amperes
- B. 0.5 amperes
- C. 2 amperes
- D. 100 amperes

**What is the current through a 24-ohm resistor connected across 240 volts?**

- A. 24,000 amperes
- B. 0.1 amperes
- C. 10 amperes
- D. 216 amperes

**What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?**

- A. 1 volt
- B. 0.25 volts
- C. 2.5 volts
- D. 1.5 volts

**What is the voltage across a 10-ohm resistor if a current of 1 ampere flows through it?**


- A. 1 volt
- B. 10 volts
- C. 11 volts
- D. 9 volts

**What is the voltage across a 10-ohm resistor if a current of 2 amperes flows through it?**

- A. 8 volts
- B. 0.2 volts
- C. 12 volts
- D. 20 volts



# Power

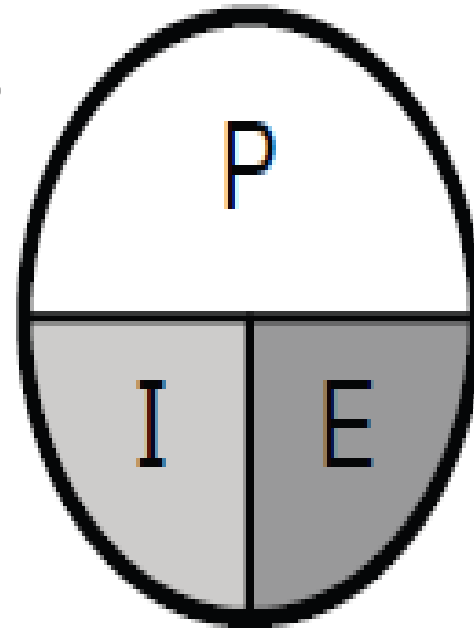

- *Power*, represented by the symbol P, is the rate at which electrical energy is used
  - Measured in *watts*  
 $P = I \times E$   
 $P \text{ (W)}$   
 $E = P / I$   
 $I = P / E$
- A device that consumes or dissipates power

Figure 3.5B — Simple diagram to help remember the Ohm's Law. If you know any two of the quantities, the equation to find the third — just cover up the unknown quantity. The positions of the remaining two symbols show if you have to multiply (side-

# Example Power Calculations

How much power is delivered by a voltage of 13.8 volts DC and a current of 10 amperes?

$$P = E \times I = 13.8 \text{ V} \times 10 \text{ A} = 138 \text{ W}$$

How much current is required to deliver 120 watts at a voltage of 12 volts DC?

$$I = P / E = 120 \text{ W} / 12 \text{ V} = 10 \text{ A}$$

# PRACTICE QUESTIONS

**Electrical power is measured in which of the following units?**

- A. Volts
- B. Watts
- C. Watt-hours
- D. Amperes

**Which term describes the rate at which electrical energy is used?**

- A. Resistance
- B. Current
- C. Power
- D. Voltage

**What is the formula used to calculate electrical power (P) in a DC circuit?**

A.  $P = I \times E$

B.  $P = E / I$

C.  $P = E - I$

D.  $P = I + E$

**How much power is delivered by a voltage of 13.8 volts DC and a current of 10 amperes?**

- A. 138 watts
- B. 0.7 watts
- C. 23.8 watts
- D. 3.8 watts

**How much power is delivered by a voltage of 12 volts DC and a current of 2.5 amperes?**

- A. 4.8 watts
- B. 30 watts
- C. 14.5 watts
- D. 0.208 watts




**How much current is required to deliver 120 watts at a voltage of 12 volts DC?**

- A. 0.1 amperes
- B. 10 amperes
- C. 12 amperes
- D. 132 amperes
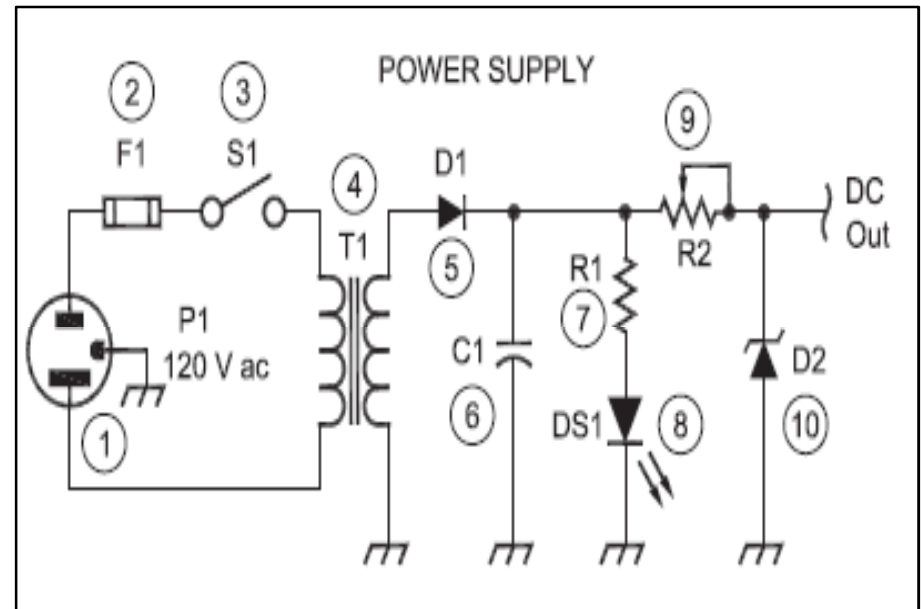
# Components and Units

- Components in electrical circuits performs functions such as storing or using energy, routing current, or amplifying signals
- The three most basic types of electronic components are resistors, capacitors and inductors





*More on schematics later ...*
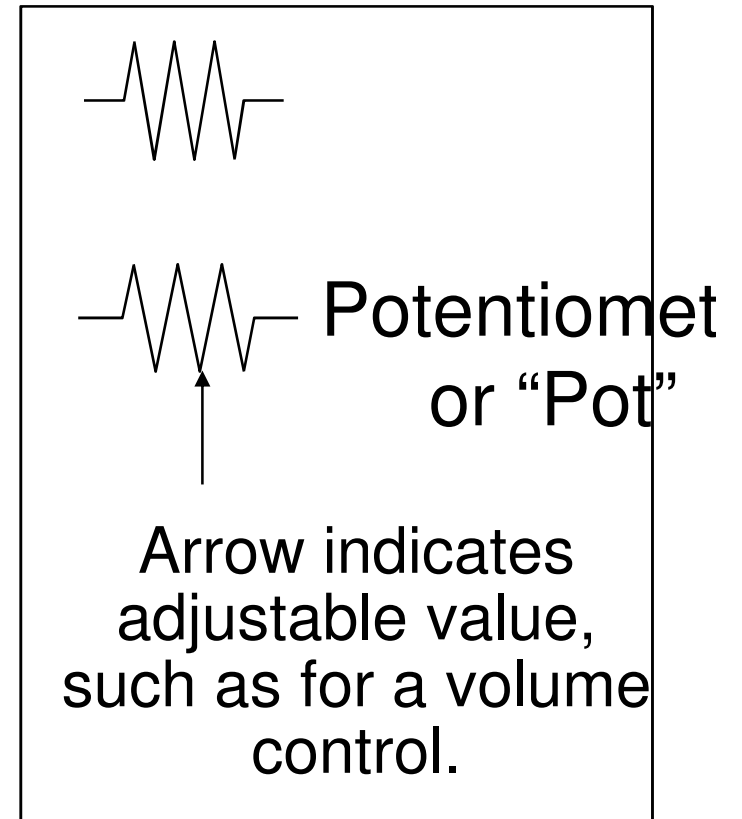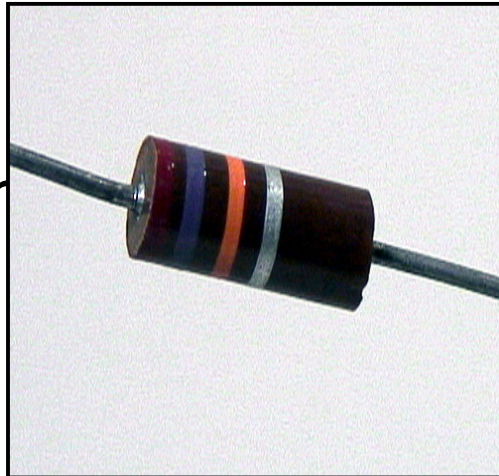
# Resistors

- Function: To restrict the flow of current, just as a valve in a water pipe restricts the flow through the pipe
- Resistance measured in ohms ( $\Omega$ )

- $I = E / R$  Remember Ohm's Law
- $E = I \times R$  Schematic
- $R = E / I$  Where



Resistor  
Schematic

# Large Variety of Resistors!





# Capacitors

- The function of a capacitor is to store electrical energy – called *capacitance*

- Schematic symbol
- Acts like a battery

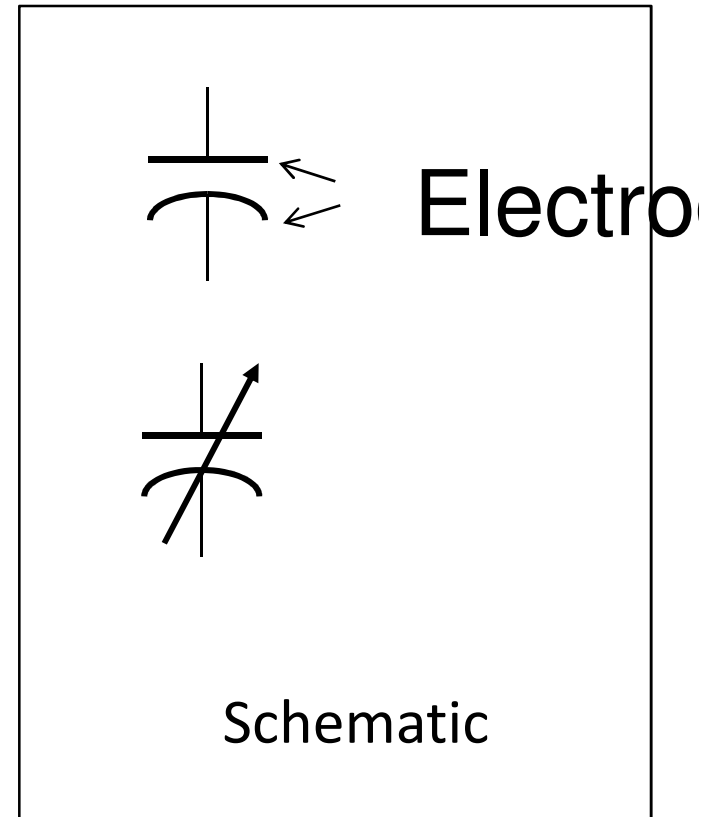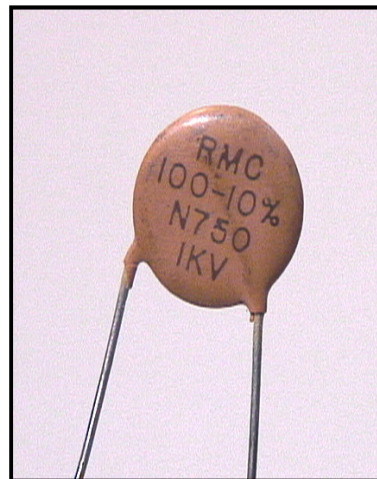*Stores energy in an electric field created by voltage between the electrodes with insulating dielectric material between*





# Capacitors (cont.)

- Store electrical energy in the *electric field* created by a voltage between two conducting surfaces or *electrodes*
- Electrodes are separated by an insulator or *dielectric*
- Storing energy this way is called *capacitance*, and it is measured in *farads* (F)


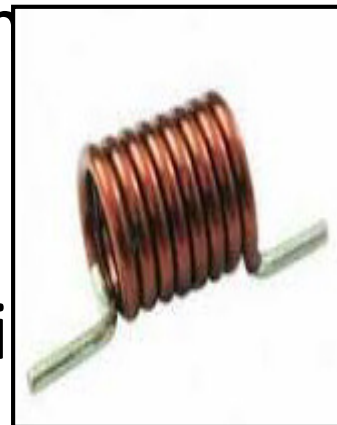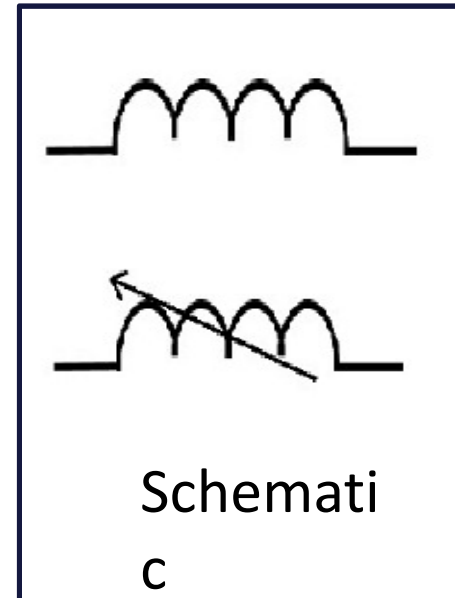
# Inductors


- Function: To store energy in the magnetic field created by current flowing in a wire
- Called *inductance*, measured in *henrys* (H)
- Made from wire wound in coil, sometimes around a core of magnetic material that concentrates the magnetic energy





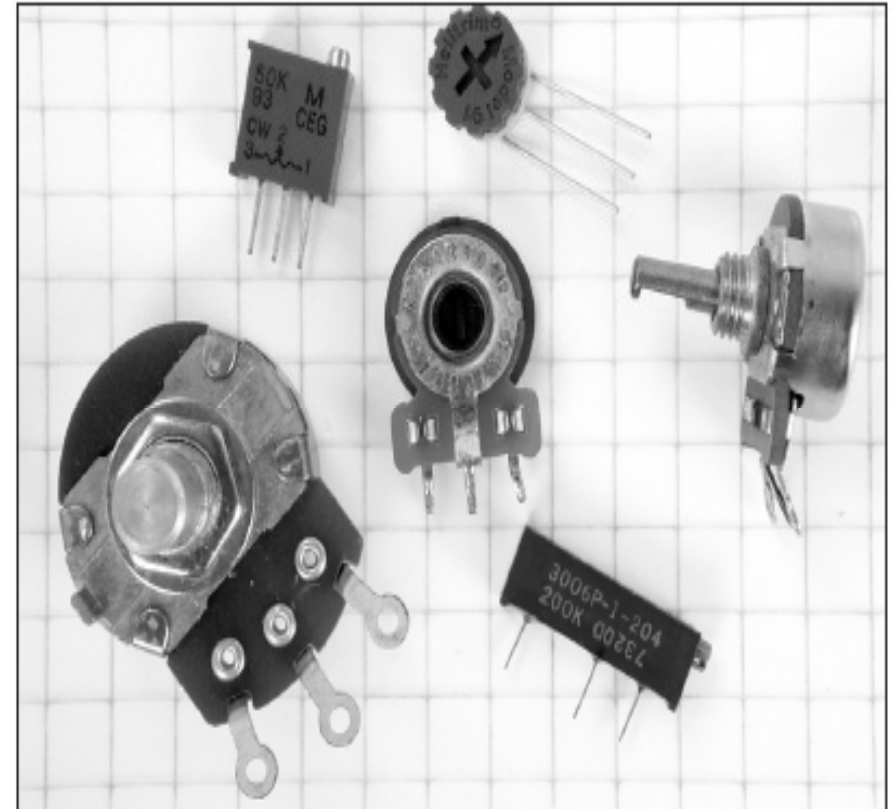
# Variable Components

- All three types of basic components are also available as adjustable or variable models
- A variable resistor is also called a *potentiometer*, frequently used to adjust voltage or potential, such as for a


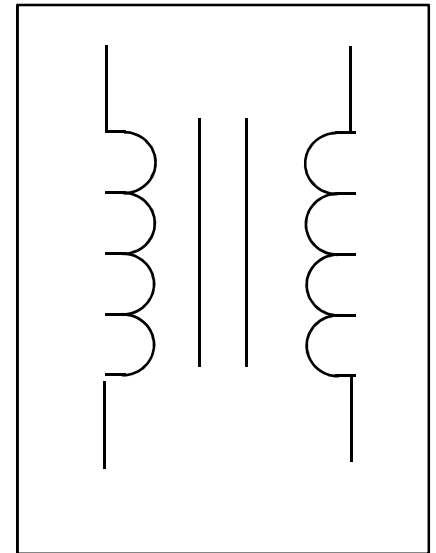
# Transformers

- Made from two or more inductors that share their stored energy
- Allows energy to be transferred from one inductor to another while changing the combination of voltage and current
- Example: A transformer is used to transfer energy



# PRACTICE QUESTIONS

**What describes the ability to store energy in an electric field?**

- A. Inductance
- B. Resistance
- C. Tolerance
- D. Capacitance

## What is the unit of capacitance?

- A. The farad
- B. The ohm
- C. The volt
- D. The henry

**What describes the ability to store energy in a magnetic field?**

- A. Admittance
- B. Capacitance
- C. Resistance
- D. Inductance

## What is the unit of inductance?

- A. The coulomb
- B. The farad
- C. The henry
- D. The ohm

**What electrical component opposes the flow of current in a DC circuit?**

- A. Inductor
- B. Resistor
- C. Inverter
- D. Transformer



**What type of component is often used as an adjustable volume control?**

- A. Fixed resistor
- B. Power resistor
- C. Potentiometer
- D. Transformer

**What electrical parameter is controlled by a potentiometer?**

- A. Inductance
- B. Resistance
- C. Capacitance
- D. Field strength

# What electrical component stores energy in an electric field?

- A. Varistor
- B. Capacitor
- C. Inductor
- D. Diode

**What type of electrical component consists of conductive surfaces separated by an insulator?**

- A. Resistor
- B. Potentiometer
- C. Oscillator
- D. Capacitor

**What type of electrical component stores energy in a magnetic field?**

- A. Varistor
- B. Capacitor
- C. Inductor
- D. Diode

**What electrical component is typically constructed as a coil of wire?**

- A. Switch
- B. Capacitor
- C. Diode
- D. Inductor

**What component changes 120 V AC power to a lower AC voltage for other uses?**

- A. Variable capacitor
- B. Transformer
- C. Transistor
- D. Diode

# Reactance and Impedance

- In a resistor, AC voltages and currents are exactly in step, or *in phase*
- In capacitors and inductors, voltage and current have a *phase difference*
- Capacitors and inductors store energy, rather than dissipating it like resistors
- Energy storage creates an effect called *reactance* (symbol  $X$ ) that acts like a resistance in opposing the flow of AC current
  - Capacitors create capacitive reactance ( $X_C$ )
  - Inductors create inductive reactance ( $X_L$ )
  - The effects of each are complementary



# Reactance and Impedance (cont.)

- The combination of *resistance* (R) and *reactance* (X) is called *impedance*, represented by the symbol Z
- Impedance represents a circuit's *opposition* to both AC and DC currents
- Radio circuits almost always have both resistance and reactance, so impedance is often used as a general term to mean the circuit's opposition to AC current flow

# PRACTICE QUESTIONS

## What is the unit of impedance?

- A. The volt
- B. The ampere
- C. The coulomb
- D. The ohm

## What is impedance?



- A. The opposition to AC current flow
- B. The inverse of resistance
- C. The Q or Quality Factor of a component
- D. The power handling capability of a component

# Resonance

- Circuits that contain both a capacitor and an inductor are called *resonant* circuits or *tuned* circuits
- A component's reactance depends on frequency
  - $X_L$  increases with frequency while  $X_C$  decreases
- At the frequency for which a circuit's  $X_L$  and  $X_C$  are *equal*, their effects cancel
  - This is the circuit's *resonant frequency*
- At *resonance*, a circuit has *only resistance*, which affects AC and DC current equally
- A tuned circuit acts as a *filter*, passing or rejecting signals at its resonant frequency
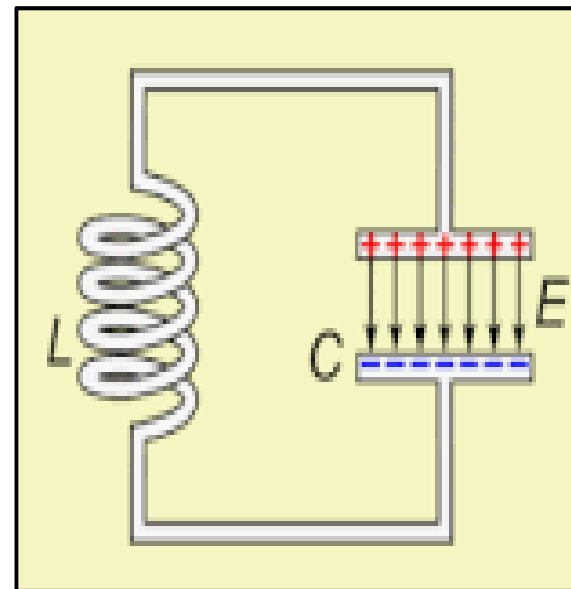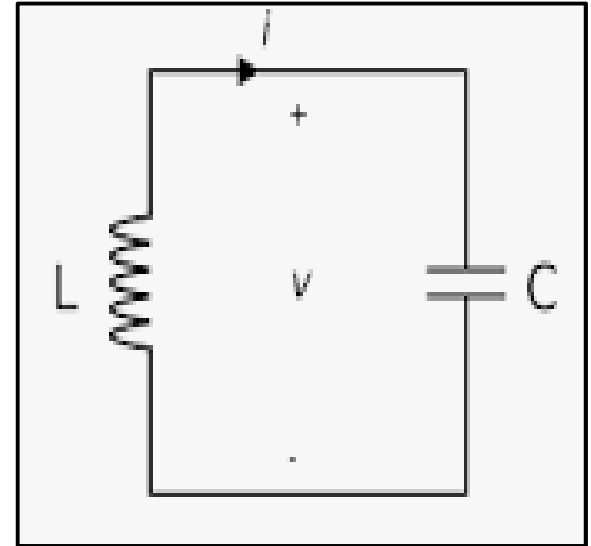
# Resonant or Tuned Circuit

- *Capacitors* and *inductors* connected together create a tuned circuit
- When  $X_L$  and  $X_C$  are equal, the circuit is resonant
- If  $C$  or  $L$  are adjustable, the resonant frequency can be varied or *tuned*



# PRACTICE QUESTIONS

**Which of the following is combined with an inductor to make a resonant circuit?**

- A. Resistor
- B. Zener diode
- C. Potentiometer
- D. Capacitor



## Which of the following is a resonant or tuned circuit?

- A. An inductor and a capacitor in series or parallel
- B. A linear voltage regulator
- C. A resistor circuit used for reducing standing wave ratio
- D. A circuit designed to provide high-fidelity audio